

# Circuits and Code

---

## CS 2130: Computer Systems and Organization 1


**Xinyao Yi** Ph.D.  
Assistant Professor

## Announcements

---

- Homework 1 due tonight
- Homework 2 available today, due next Monday

## Another Counter

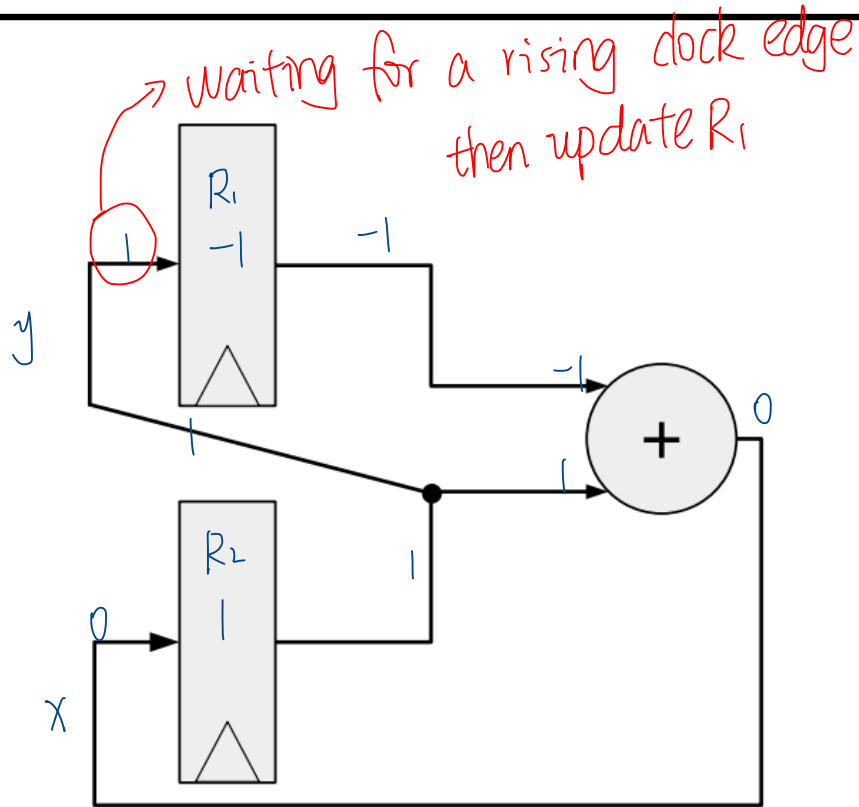


clock	$x$	$y$	$R_1$	$R_2$
0	0	1	-1	1
1	1	0	1	0
2	1	1	0	1
3	2	1	1	1
4	3	2	1	2
5	5	3		

$x$  : Fibonacci sequence.

## Common Model in Computers

---

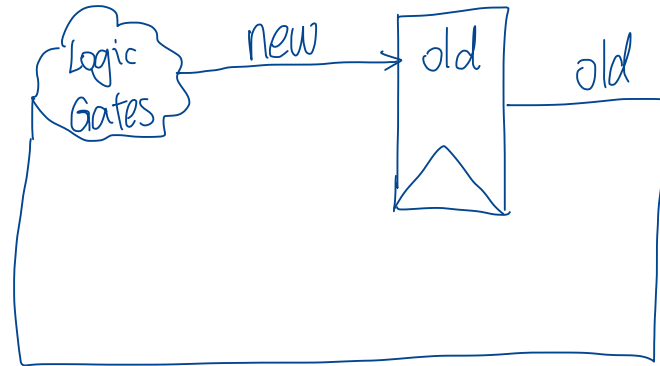

The register ignore  
all the calculations/updates  
until rising clock edge.

## Code to Build Circuits from Gates

---

Write code to build circuits from gates

- Gates we already know:  $\&$ ,  $|$ ,  $\wedge$ ,  $\sim$
- Operations we can build from gates:  $+$ ,  $-$
- Others we can build:


$$\begin{array}{r} * : 2130 \\ \times 1101 \\ \hline 2130 \\ 0000 \\ 2130 \\ 2130 \end{array} \quad \text{(left shift and add)}$$

## Code to Build Circuits from Gates

---

Write code to build circuits from gates

- Gates we already know:  $\&$ ,  $|$ ,  $\wedge$ ,  $\sim$
- Operations we can build from gates:  $+$ ,  $-$
- Others we can build:
- Ternary operator:  $?:$   $a == 0 ? b : c$

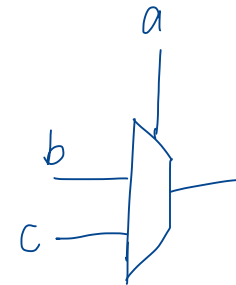


## Equals

---

Equals: =

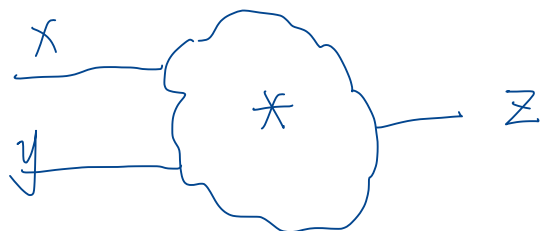- Attach with a wire (i.e., connect things)
- Ex:  $z = x * y$



attaching the circuit to  
whatever I'm trying to output

## Equals


---

Equals: =

- Attach with a wire (i.e., connect things)
- Ex:  $z = x * y$
- What about the following?

$x = 1$

$x = 0$

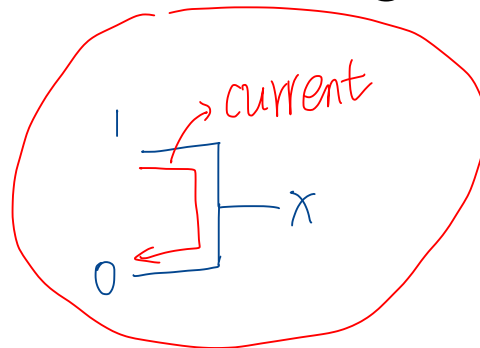

doesn't work!



## Equals

---

Equals: =

- Attach with a wire (i.e., connect things)
- Ex:  $z = x * y$
- What about the following?  
 $x = 1$   
 $x = 0$
- **Single assignment:** each variable can only be assigned a value once